

# Lab 1

Madiba Hudson-Quansah

### Question 1

1. Complete the truth table for R and C as a function of  $Q_1$ ,  $Q_2$ ,  $Q_3$ , and  $X$
2. Complete the state table based on the state transition diagram as above.

**Solution:**

1.

$Q_1$	$Q_2$	$Q_3$	$X$	Total Amount	Temp	$R$	$C$
0	0	0	0	\$0.00	00	0	0
0	0	0	1	\$0.00	00	0	0
0	0	1	0	\$0.25	01	0	0
0	0	1	1	\$0.25	01	0	0
0	1	0	0	\$0.25	01	0	0
0	1	0	1	\$0.25	01	0	0
0	1	1	0	\$0.50	10	0	0
0	1	1	1	\$0.50	10	1	0
1	0	0	0	\$0.25	01	0	0
1	0	0	1	\$0.25	01	0	0
1	0	1	0	\$0.50	10	0	0
1	0	1	1	\$0.50	10	1	0
1	1	0	0	\$0.50	10	0	0
1	1	0	1	\$0.50	10	1	0
1	1	1	0	\$0.75	11	1	1
1	1	1	1	\$0.75	11	1	0

2.

Present State	$Q_1$	$Q_2$	$Q_3$	$X$	Next State	$R$	$C$
S0	0	0	0	0	S0	0	0
S0	0	0	1	0	S1	0	0
S0	0	1	0	0	S1	0	0
S0	1	0	0	0	S1	0	0
S0	0	0	1	1	S1	0	0
S0	0	1	0	1	S1	0	0
S0	1	0	0	1	S1	0	0
S1	0	0	1	0	S2	0	0
S1	0	1	0	0	S2	0	0
S1	1	0	0	0	S2	0	0
S1	0	0	1	1	S2	1	0
S1	0	1	0	1	S2	1	0
S1	1	0	0	1	S2	1	0
S2	0	0	1	0	S3	1	0
S2	0	1	0	0	S3	1	0
S2	1	0	0	0	S3	1	0
S2	0	0	1	1	S3	1	1
S2	0	1	0	1	S3	1	1
S2	1	0	0	1	S3	1	1
S3	1	0	0	0	S3	1	0
S3	0	0	1	1	S3	1	1
S3	0	1	0	1	S3	1	1
S3	1	0	0	1	S3	1	1

		$Q_3 X$			
		00	01	11	10
$Q_1 Q_2$	00	0	0	0	0
	01	0	0	1	1
	11	1	1	1	1
	10	0	0	1	1

Figure 1:  $D_1$

3.

$$D_1 = Q_1 Q_2 + Q_2 Q_3 + Q_1 Q_3$$

		$Q_3 X$			
		00	01	11	10
$Q_1 Q_2$	00	0	0	1	1
	01	1	1	0	0
	11	0	0	1	1
	10	1	1	0	0

Figure 2:  $D_0$

$$\begin{aligned}
 D_0 &= \overline{Q_1} \overline{Q_2} Q_3 + \overline{Q_1} Q_2 \overline{Q_3} + Q_1 Q_2 Q_3 + Q_1 \overline{Q_2} \overline{Q_3} \\
 &= Q_1 \oplus Q_2 \oplus Q_3
 \end{aligned}$$

## Question 2

Xilinx Vivado

**Solution:**

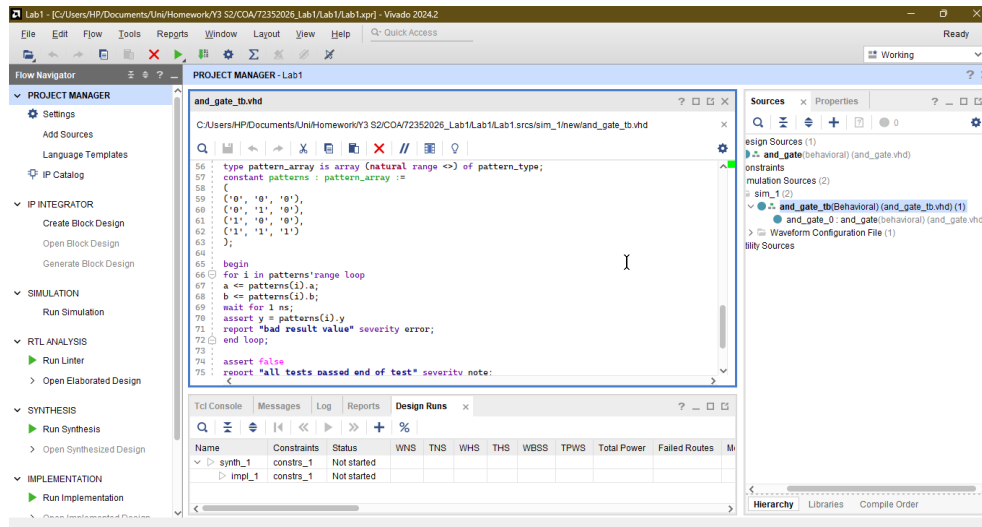


Figure 3: Test Bench

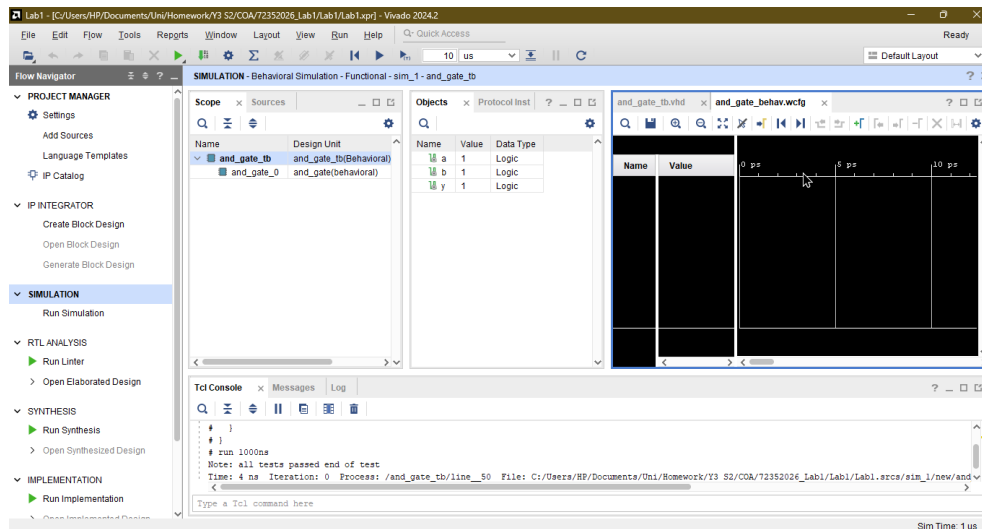


Figure 4: Test Bench Behavioural simulation

### Question 3

What assumptions did you make while designing the vending machine coin counter? Were these assumptions realistic and clearly justified?

#### Solution:

- Coin Slots are independent - Each slot is independent of the other and the machine does not check which specific slot the quarters were placed in only the total amount. This is a realistic assumption as this reflects how real vending machines work.
- Change is limited to 1 quarter - The machine only returns 1 quarter as change. This is an assumption to keep the design simple and easy to implement.
- Slots only accept valid quarters - Only valid U.S. quarters are accepted by the machine. This is a realistic assumption as the machine is designed to accept only quarters.

#### Question 4

How did you decide the outputs for R (release soda) and C (return change)? Could there be alternative conditions or approaches to achieve the same functionality?

**Solution:** The outputs for R and C were decided based on the total amount of money given to the machine and the soda chosen by the user. The machine releases a soda if the total amount is greater than or equal to the cost of the soda. An alternative implementation could be to have the machine release a soda if the total amount is greater than the cost of the soda by a certain amount. This would allow the machine to release a soda even if the user gives more money than required for the soda.

#### Question 5

While creating the state table, how did you ensure all possible transitions were accounted for? Were there any ambiguous or conflicting states that required special handling?

**Solution:** I ensured all possible transitions were accounted for by creating a state transition diagram and then creating a state table based on the diagram. I made sure to include all possible states and transitions in the state table. There were no ambiguous or conflicting states that required special handling.

#### Question 6

What were the key challenges you faced during the installation of Xilinx Vivado? Were there any system requirements or errors you needed to address?

**Solution:** I faced no challenges during the installation of Xilinx Vivado.

#### Question 7

How would you explain the importance of hardware description languages (like VHDL) in modern digital design to someone unfamiliar with the field?

**Solution:** Hardware description languages serve as a way to describe the behaviour of digital circuits in a way that is easily understood by both humans and computers. They allow designers to create complex digital circuits without having to worry about the low-level details of the hardware. This makes it easier to design, test, and debug digital circuits and allows for faster development times.